

UNIVERSITY OF THE WEST INDIES  
CAVE HILL CAMPUS

*Department of Computer Science, Mathematics & Physics*

**ELET1210 - Digital Electronics 1**

**Class Test 2**

**Thursday, December 2, 2021**

1. 01010110 is passed through a parity checker and the output is 1.  
Is this an EVEN or ODD parity system? [1]

2. How many flip-flops will be complemented when the counter below is incremented  
01100111 [1]

3. Which Logic Family has the shortest Propagation Delay? [1]

4. Implement the following function using a 3 x 8 decoder and one additional logic gate

$$F = (A + \bar{B})(B + C) \quad [3]$$

5. Implement the following function using a 4 x 1 multiplexer

$$F = \bar{A}\bar{C} + BC + ABC \quad [4]$$

EITHER DO QUESTION 6 OR QUESTION 7 BUT NOT BOTH

6. A 3-bit finite state device, built with J-K flip flops, has the following flip-flop input functions

$$\begin{array}{ll} J_A = \bar{B} + ABC & K_A = 1 \\ J_B = C & K_B = \bar{A}B + A\bar{B}\bar{C} + \bar{A}B\bar{C} \\ J_C = A\bar{B} & K_C = \bar{B} + A \end{array}$$

Draw the State Diagram and find the State Equations

What are the unused states?

Is the device self-correcting? [15]

7. A 3-bit finite state device, built with J-K flip flops, has the following repeating sequence

2,1,7,3,5.....

Find the simplified flip flop input functions and analyze the unused state behavior

Draw the State Diagram [15]